## **Practice problems for chapter 25: Capacitance**

•1 The two metal objects in Fig. 25-24 have net charges of +70 pC and -70 pC, which result in a 20 V potential difference between them. (a) What is the capacitance of the system? (b) If the charges are changed to +200 pC and -200 pC, what does the capacitance become? (c) What does the potential difference become?



- •3 SSM A parallel-plate capacitor has circular plates of 8.20 cm radius and 1.30 mm separation. (a) Calculate the capacitance. (b) Find the charge for a potential difference of 120 V.
- •4 The plates of a spherical capacitor have radii 38.0 mm and 40.0 mm. (a) Calculate the capacitance. (b) What must be the plate area of a parallel-plate capacitor with the same plate separation and capacitance?
- •5 What is the capacitance of a drop that results when two mercury spheres, each of radius R = 2.00 mm, merge?
- ••14 •• In Fig. 25-30, the battery has a potential difference of V = 10.0 V and the five capacitors each have a capacitance of  $10.0 \mu\text{F}$ . What is the charge on (a) capacitor 1 and (b) capacitor 2?
- ••15 •• In Fig. 25-31, a 20.0 V battery is connected across capacitors of capacitances  $C_1 = C_6 = 3.00 \,\mu\text{F}$

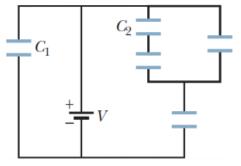


Figure 25-30 Problem 14.

and  $C_3 = C_5 = 2.00C_2 = 2.00C_4 = 4.00 \,\mu\text{F}$ . What are (a) the equivalent capacitance  $C_{\text{eq}}$  of the capacitors and (b) the charge stored by  $C_{\text{eq}}$ ? What are (c)  $V_1$  and (d)  $q_1$  of capacitor 1, (e)  $V_2$  and (f)  $q_2$  of capacitor 2, and (g)  $V_3$  and (h)  $q_3$  of capacitor 3?

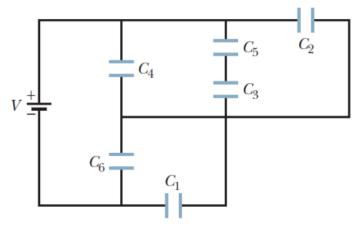


Figure 25-31 Problem 15.

**••21 SSM WWW** In Fig. 25-36, the capacitances are  $C_1 = 1.0 \,\mu\text{F}$  and  $C_2 = 3.0 \,\mu\text{F}$ , and both capacitors are charged to a potential difference of  $V = 100 \,\text{V}$  but with opposite polarity as shown. Switches  $S_1$  and  $S_2$  are now closed. (a) What is now the po-

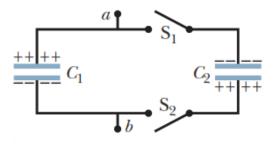


Figure 25-36 Problem 21.

tential difference between points a and b? What now is the charge on capacitor (b) 1 and (c) 2?